

University of Saskatchewan
Department of Electrical and Computer Engineering
EE 241 - Introduction to Electric Power Systems
Midterm Examination
February 13, 2019

Instructor: S.O. Faried

Duration: 2 hours

1. The following four loads are connected in parallel and supplied from a single-phase 600 V, 60-Hz source:
Load A: 20 kVA, p.f. 0.5 lagging
Load B: 10 kW, p.f. 0.9 leading
Load C: 20 kVA, 12 kVAR lagging
Load D: 10 kW, 10 kVA
 - (a) Draw the power triangle of the total load indicating the values of P, Q, S and the phase angle ϕ .
 - (b) Determine the kVAR of a capacitor installed to improve the power factor to 0.95 lagging.
 - (c) What is the value of the capacitor capacitance in μF .

(7 Marks)
2. A three-phase, **three-wire**, 208 V, ABC system supplies a Y-connected load in which $Z_A = Z_B = Z_C = 10\angle 30^\circ \Omega$ and a single-phase load $Z_{AB} = 30\angle 30^\circ \Omega$ as shown in Figure 1. Find the wattmeter reading.

*Happy
Valentine's
Day*

***You are at the wrong
place. I am not Figure 1***



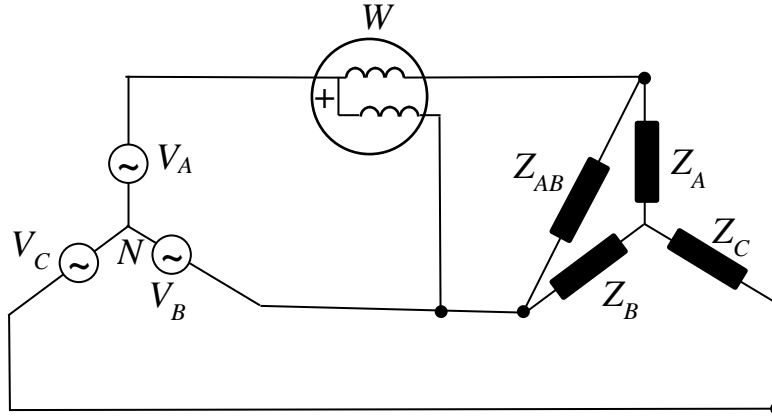


Figure 1.

(6 Marks)

3. A three-phase, **three-wire**, 380 V, ABC system supplies a Y-connected load of $Z_A = 10\angle 0^\circ \Omega$, $Z_B = 15\angle 60^\circ \Omega$, $Z_C = 10\angle -30^\circ \Omega$ through a three-phase cable with impedance $Z_{Cable} = 1\angle 75^\circ \Omega$ as shown in Figure 2. Find:

- The load phase voltages V_{LA}, V_{LB}, V_{LC} . Express the values in polar form (*Magnitude* \angle *angle* $^\circ$).
- The sum of the line-to-line voltages at the load ($V_{LAB}, V_{LBC}, V_{LCA}$).
- The total active power loss in the cable.

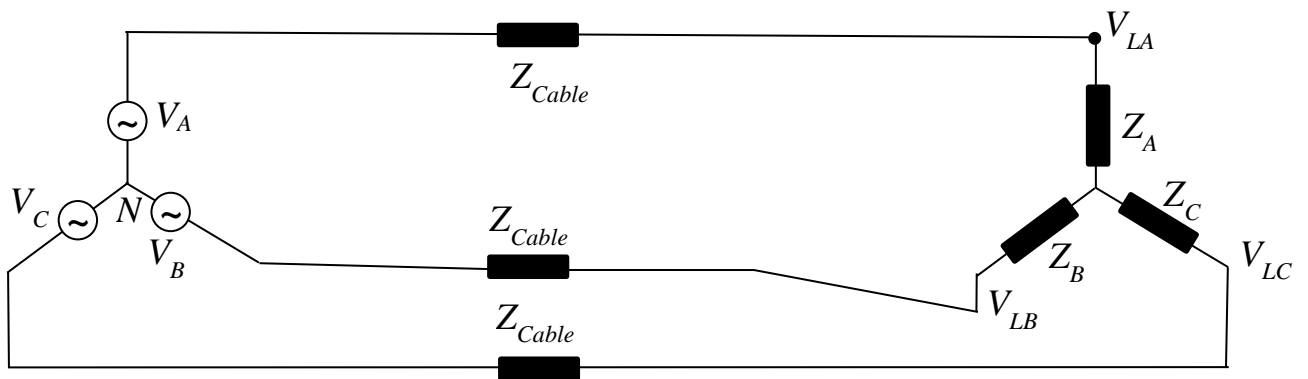


Figure 2.

(7 Marks)

Question # 1

1-a

$$P = |S| \cos \phi$$

$$Q = |S| \sin \phi$$

$$\frac{Q}{P} = \tan \phi$$

$$P.F. = \cos \phi$$

Load	P, KW	Q, KVAR
A	10	17.3205
B	10	-4.8432
C	16	12
D	10	0

$$\text{Load B: } \phi = \cos^{-1} 0.9 = 25.8419^\circ \Rightarrow |S| = \frac{P}{\cos \phi} = 11.1111 \text{ VA}$$

$$Q = |S| \sin \phi = \text{KVAR}$$

$$\text{Load C: } 12 = 20 \sin \phi \Rightarrow \phi = 36.8699^\circ$$


$$P = 20 \cos \phi =$$

$$P_T = 46 \text{ KW}$$

$$Q_T = 24.4773 \text{ KVAR}$$

$$\phi = 28.0181^\circ$$

$$|S_T| = \sqrt{(46)^2 + (24.477)^2} = 52.1027 \text{ KVA}$$

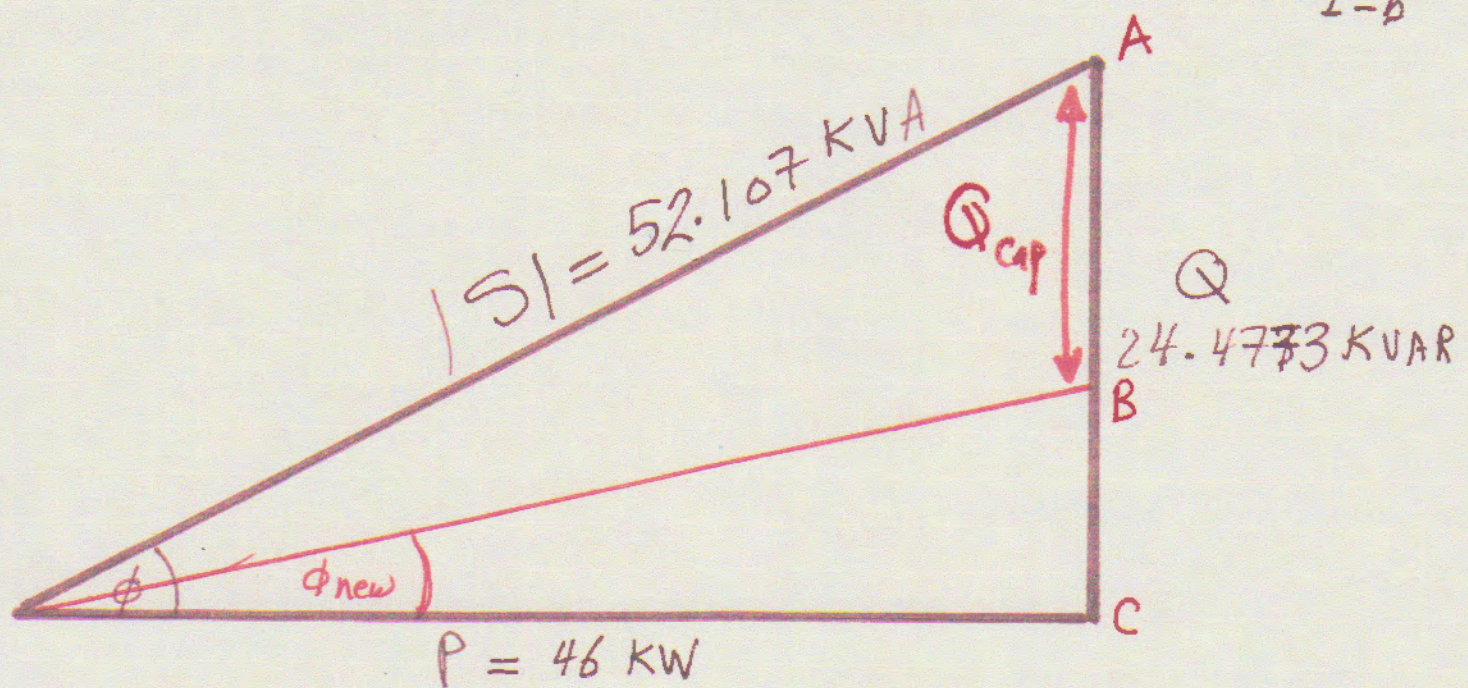


$$\phi_{\text{new}} = \cos^{-1} 0.95 = 18.1949^\circ$$

$$Q_{\text{capacitor}} = 24.4773 - 46 \tan \phi_{\text{new}} = \overline{AB}$$

$$Q_{\text{capacitive}} = 9.3578 \text{ KVAR}$$

$$Q_{\text{cap}} = |I|^2 |X_c| \text{ and } |I| = \frac{|V|}{|X_c|}$$

$$Q_{\text{cap}} = \frac{|V|^2}{|X_c|}$$

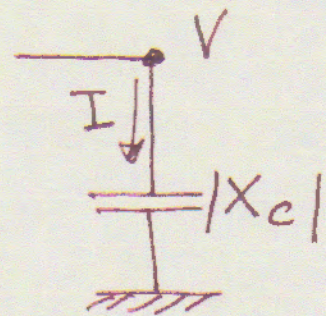

$$9357.8312 = \frac{(600)^2}{|X_c|}$$


$$|X_c| = 38.4705 \quad \omega = \frac{1}{2\pi \times 60 \text{ C}}$$

$$C = 68.9512 \text{ }\mu\text{F}$$

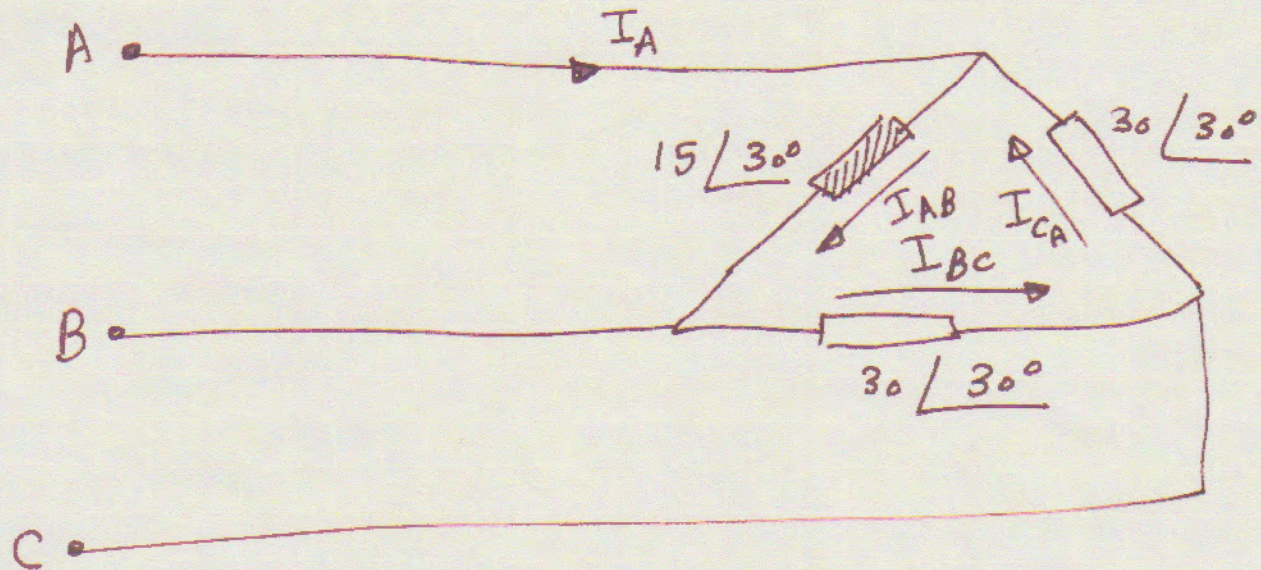Question # 2

2-9

Convert the Y to $\Delta \Rightarrow Z_{\Delta} = 10 \angle 30^{\circ} + 10 \angle 30^{\circ} + \frac{10 \angle 30^{\circ} \cdot 10 \angle 30^{\circ}}{10 \angle 30^{\circ}}$
 $Z_{\Delta} = 30 \angle 30^{\circ} \Omega$



$$V_{AB} = 208 \angle 0^{\circ} \text{ V}$$

$$V_{BC} = 208 \angle -120^{\circ} \text{ V}$$

$$V_{CA} = 208 \angle 120^{\circ} \text{ V}$$

$$I_{AB} = \frac{V_{AB}}{15 \angle 30^{\circ}} = \frac{208 \angle 0^{\circ}}{15 \angle 30^{\circ}} = 13.8667 \angle -30^{\circ} \text{ A}$$

$$I_{BC} = \frac{208 \angle -120^{\circ}}{30 \angle 30^{\circ}} = 6.9333 \angle -150^{\circ} \text{ A}$$


$$I_{CA} = \frac{208 \angle 120^{\circ}}{30 \angle 30^{\circ}} = 6.9333 \angle 90^{\circ} \text{ A}$$

$$I_A + I_{CA} = I_{AB} \Rightarrow I_A = I_{AB} - I_{CA}$$

$$I_A = 13.8667 \angle -30^\circ - 6.9333 \angle 90^\circ$$

$$I_A = 18.3439 \angle -49.1065^\circ \text{ A}$$
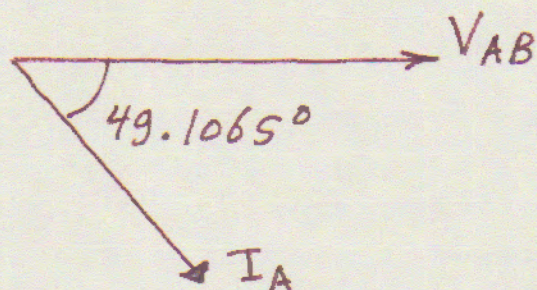
$$V_{AB} = 208 \angle 0^\circ \text{ Reference}$$




$$W_{\text{Reading}} = |V_{AB}| |I_A| \cos \angle V_{AB} I_A$$

$$= 208 * 18.3439 \cos 49.1065^\circ$$

$$W_{\text{Reading}} = 2.4979 \text{ KW}$$

Question # 3

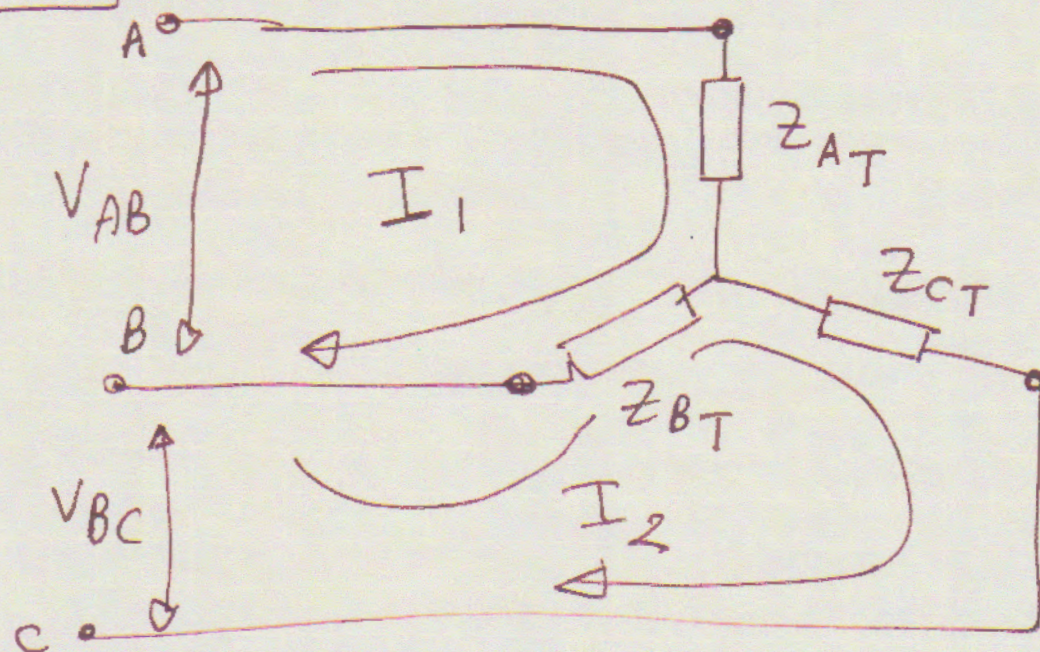

$$Z_{AT} = 10 \angle 0^\circ + 1 \angle 75^\circ = 10.3042 \angle 5.3789^\circ \Omega$$

$$Z_{BT} = 15 \angle 60^\circ + 1 \angle 75^\circ = 15.968 \angle 60.9287^\circ \Omega$$

$$Z_{CT} = 10 \angle -30^\circ + 1 \angle 75^\circ = 9.789 \angle -24.3371^\circ \Omega$$


$$V_{AB} = 380 \angle 0^\circ \text{ V}$$

$$V_{BC} = 380 \angle -120^\circ \text{ V}$$

$$V_{AB} - Z_{AT} I_1 - Z_{BT} I_1 + I_2 Z_{BT} = 0$$

$$V_{AB} = I_1 (Z_{AT} + Z_{BT}) - I_2 Z_{BT}$$
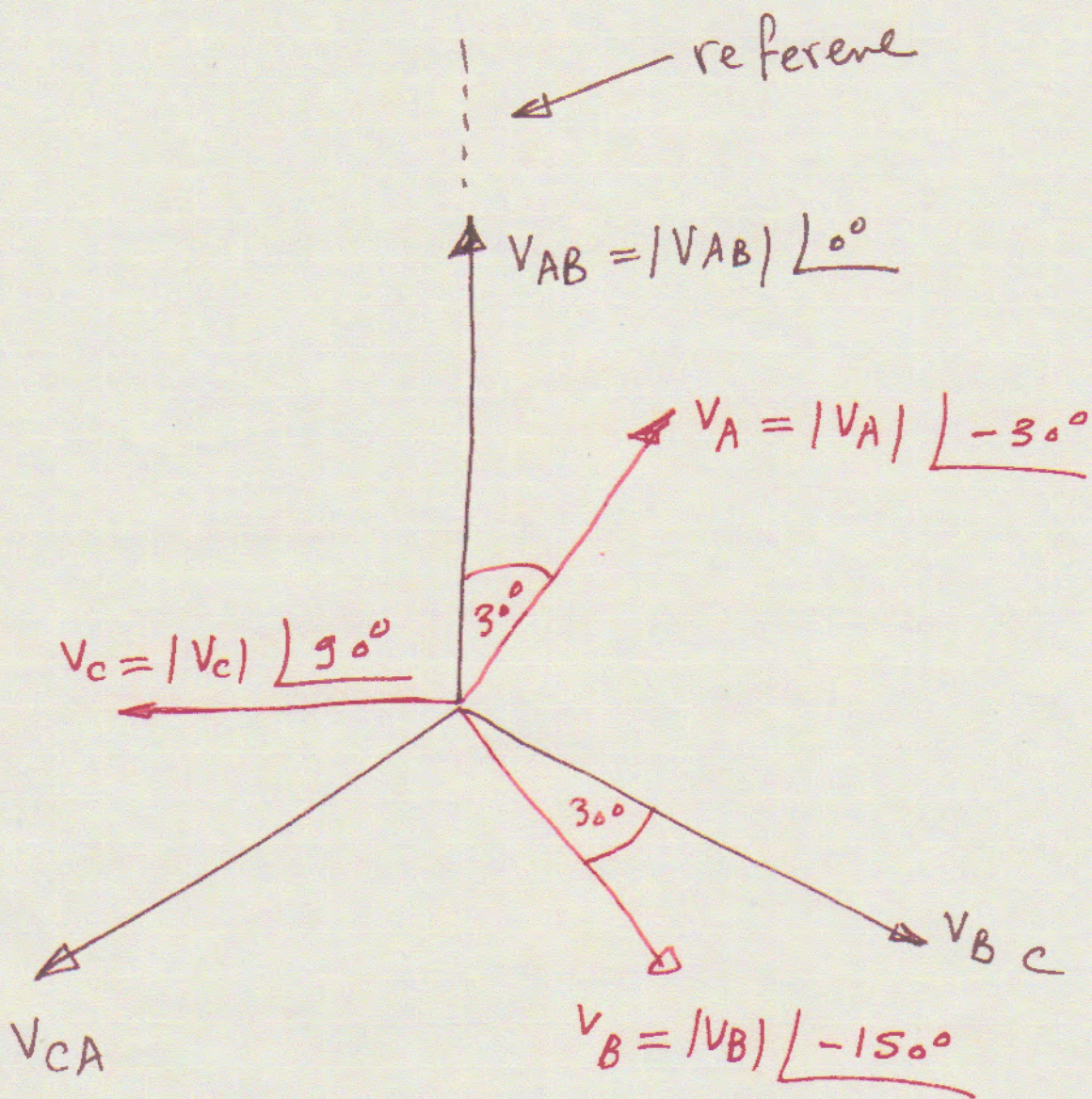
$$V_{BC} - I_2 Z_{BT} - I_2 Z_{CT} + I_1 Z_{BT} = 0$$



$$V_{BC} = -I_1 z_{BT} + I_2 (z_{BT} + z_{CT})$$

$$\begin{bmatrix} 23.3946 \angle 39.6316^\circ & -15.968 \angle 60.9287^\circ \\ -15.968 \angle 60.9287^\circ & 19.4063 \angle 30.7497^\circ \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 380 \angle 0^\circ \\ 380 \angle -12^\circ \end{bmatrix}$$

$$\Delta = 356.2741 \angle 36.3318^\circ \quad \Omega \quad \checkmark$$

$$I_1 = \frac{\Delta_1}{\Delta}, \quad I_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta_1 = \begin{vmatrix} 380 \angle 0^\circ & -15.968 \angle 60.9287^\circ \\ 380 \angle -12^\circ & 19.4063 \angle 30.7497^\circ \end{vmatrix}$$

$$\Delta_1 = 9,564.5156 \angle -8.6264^\circ \quad \checkmark$$

$$I_1 = 26.8459 \angle -44.9582^\circ \text{ A}$$

$$\Delta_2 = \begin{vmatrix} 23.3946 \angle 39.6316^\circ & 380 \angle 0^\circ \\ -15.968 \angle 60.9287^\circ & 380 \angle -120^\circ \end{vmatrix}$$

$$\Delta_2 = 5626.3751 \angle -37.9652^\circ$$

$$I_2 = 15.7923 \angle -74.297^\circ \text{ A}$$

$$I_A = 26.8459 \angle -44.9582^\circ \text{ A}$$


$$I_B = 15.1967 \angle 165.6508^\circ \text{ A}$$

$$I_C = -15.7923 \angle -74.297^\circ \text{ A}$$

$$Z_{\text{able}} = 1 \angle 75^\circ = 0.2588 + j 0.9659 \Omega$$

$$P_{\text{loss}} = (26.8459)^2 * 0.2588 + (15.1967)^2 * 0.2588 \\ + (15.7923)^2 * 0.2588$$

$$P_{\text{loss}} = 310.8288 \text{ W}$$

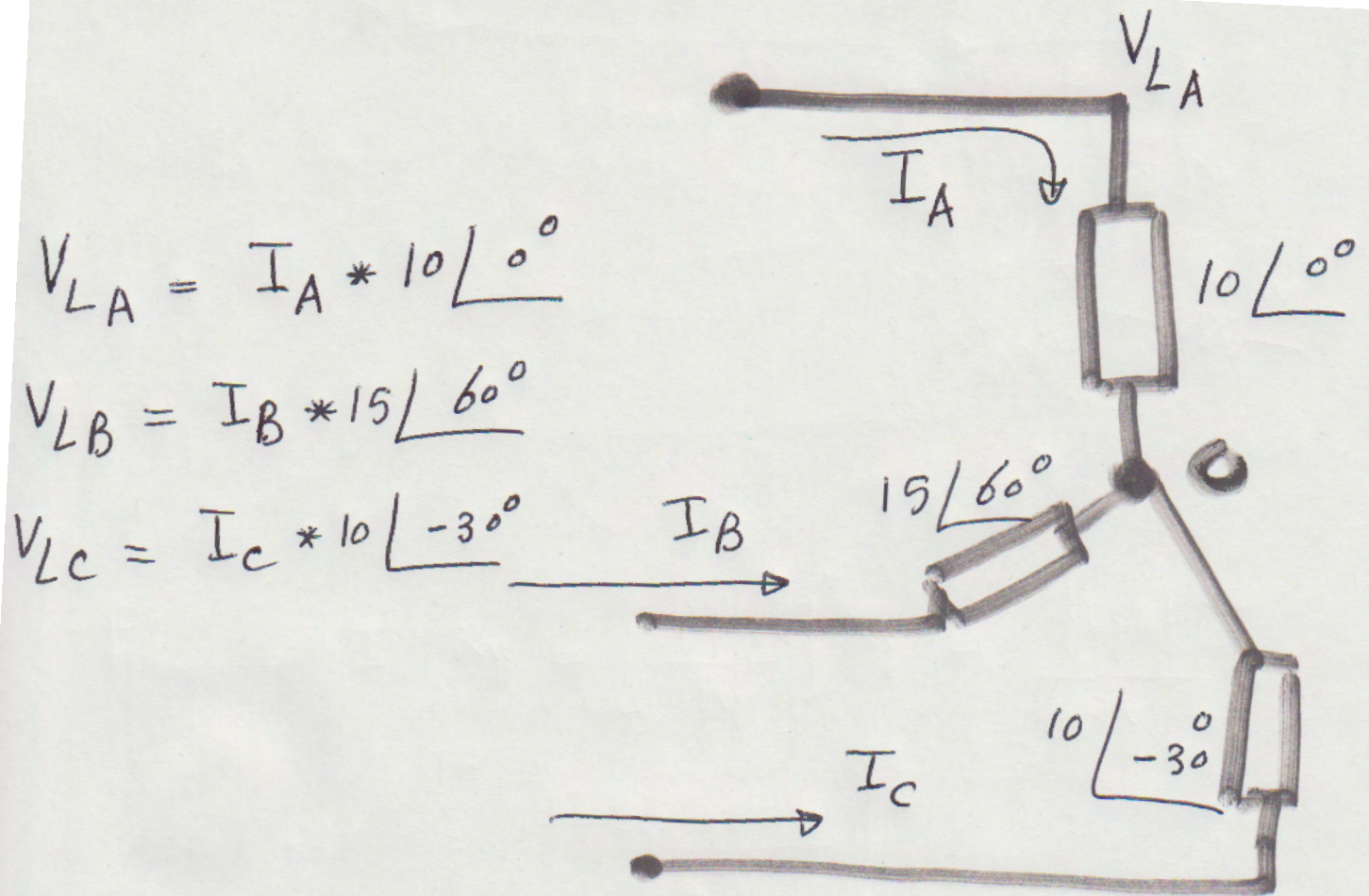

$$V_{LA} = 268.459 \angle -44.9582^\circ \text{ V}$$

$$V_{LB} = 227.9505 \angle -134.3492^\circ \text{ V}$$

$$V_{LC} = 151.967 \angle 75.703^\circ \text{ V}$$

Line-to-Line voltages at the load

$$V_{LAB} = V_{LA} - V_{LB} = 350.3295 \angle -4.3685^\circ \text{ V}$$

$$V_{LBC} = V_{LB} - V_{LC} = 367.4557 \angle -122.3962^\circ \text{ V}$$

$$V_{LCA} = V_{LC} - V_{LA} = 369.8295 \quad \underline{114.3424^\circ} \text{ V}$$

$$V_{LAB} + V_{LBC} + V_{LCA} = 0$$

The sum of the line-to-line voltages
is always zero (balanced or unbalanced)
load